



భారతీయ సాంకేతిక విజ్ఞాన సంస్థ హైదరాబాద్  
भारतीय प्रौद्योगिकी संस्थान हैदराबाद  
Indian Institute of Technology Hyderabad

## EE1200 - ELECTRIC CIRCUITS LAB

### Experiment-9

EE24BTECH11012 - Bhavanisankar G S  
EE24BTECH11019 - Dwarak A

April 13, 2025

## Contents

<b>1</b>	<b>Aim</b>	<b>3</b>
<b>2</b>	<b>Apparatus Required</b>	<b>3</b>
<b>3</b>	<b>Theory</b>	<b>3</b>
<b>4</b>	<b>State diagram</b>	<b>4</b>
<b>5</b>	<b>State transition table</b>	<b>4</b>
<b>6</b>	<b>Circuit diagram</b>	<b>5</b>
<b>7</b>	<b>Procedure</b>	<b>5</b>
<b>8</b>	<b>Observation</b>	<b>6</b>
<b>9</b>	<b>Result</b>	<b>7</b>

## 1 Aim

The objective of this experiment is to build a sequence detector, that detects the sequence of **11011** by using a **Moore machine** .

## 2 Apparatus Required

- 7474 D flip-flops
- 7432 2-input OR gates
- 7411 3-input AND gates
- LED
- Connecting wires
- Breadboard
- An Arduino UNO
- Resistor (  $220\Omega$  )

## 3 Theory

A Moore machine is a finite-state machine where the output depends solely on the current state. Key characteristics include:

- **States:** A finite set of states.
- **Input Alphabet:** A set of input symbols.
- **Output Alphabet:** A set of output symbols.
- **State Transition Function:** Maps current state and input to the next state.
- **Output Function:** Maps current state to an output symbol.

Formally, a Moore machine is defined as:

$$M = (Q, \Sigma, \Lambda, \delta, \omega, q_0)$$

where  $Q$  is the set of states,  $\Sigma$  is the input alphabet,  $\Lambda$  is the output alphabet,  $\delta$  is the state transition function,  $\omega$  is the output function, and  $q_0$  is the initial state.

### Advantages:

- Simplicity and stability in output.
- Useful in digital circuit design and control systems.

### Disadvantages:

- May require more states compared to Mealy machines.
- Output changes occur one clock cycle after state change.

## 4 State diagram

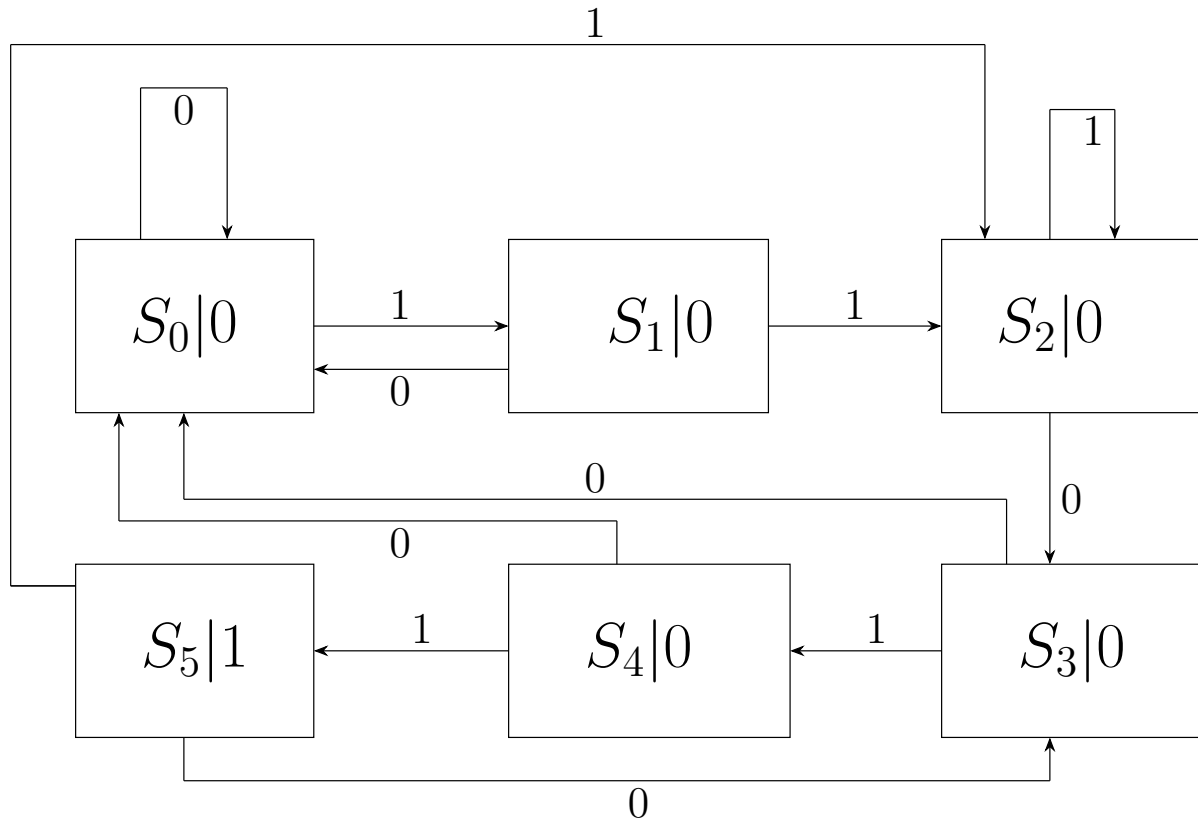


Figure 1: State Diagram

## 5 State transition table

- The given sequence, **11011** has 5 bits. Hence, the required number of states is 6 and the required number of flip-flops to implement this circuit is three.
- Let us assign the following binary values to each state -
- The state-transition table using T flip-flops is given below.
- The corresponding logic is given below -
- The state transition table using D flip-flops is given below -

State	Binary value
$S_0$	000
$S_1$	001
$S_2$	011
$S_3$	010
$S_4$	110
$S_5$	111

Table 1: State values

Input	$P_2$	$P_1$	$P_0$	$T_2$	$T_1$	$T_0$	$N_2$	$N_1$	$N_0$	Output
0	0	0	0	0	0	0	0	0	0	0
1	0	0	0	0	0	1	0	0	1	0
0	0	0	1	0	0	1	0	0	0	0
1	0	0	1	0	1	0	0	1	1	0
0	0	1	1	0	0	1	0	0	1	0
1	0	1	1	0	0	0	0	1	1	0
0	0	1	0	0	1	0	0	0	0	0
1	0	1	0	1	0	0	1	1	0	0
0	1	1	0	1	1	0	0	0	0	0
1	1	1	0	0	0	1	1	1	1	0
0	1	1	1	1	0	1	0	1	0	1
1	1	1	1	1	0	0	0	1	1	1
0	1	0	0	X	X	X	X	X	X	X
1	1	0	0	X	X	X	X	X	X	X
0	1	0	1	X	X	X	X	X	X	X
0	1	0	1	X	X	X	X	X	X	X

Table 2: State transition table - T flip-flops

- The corresponding logic is given below -
- From 3 and 5, it can be seen that using a D flip-flop minimizes the circuit complexity, and hence we shall adopt that.

## 6 Circuit diagram

## 7 Procedure

- Connect the circuit according to the figure 2.
- When the circuit reaches the  $S_5$ , the LED glows.
- The number of times the sequence **11011** appears can be found out by noting the number of times the LED lights up.

State	Logic
$T_2$	$Q_2Q_0 + \bar{I}Q_2 + I\bar{Q}_2Q_1\bar{Q}_0$
$T_1$	$\bar{Q}_1Q_0I + Q_1Q_0\bar{I}$
$T_0$	$Q_0\bar{I} + \bar{Q}_1Q_0I + I\bar{Q}_2Q_0$
$O$	$Q_0Q_1Q_2$

Table 3: Logic - T flip-flops

Input	$P_2$	$P_1$	$P_0$	$D_2$	$D_1$	$D_0$	$N_2$	$N_1$	$N_0$	Output
0	0	0	0	0	0	0	0	0	0	0
1	0	0	0	0	0	1	0	0	1	0
0	0	0	1	0	0	0	0	0	0	0
1	0	0	1	0	1	1	0	1	1	0
0	0	1	1	0	0	1	0	0	1	0
1	0	1	1	0	1	1	0	1	1	0
0	0	1	0	0	0	0	0	0	0	0
1	0	1	0	1	1	0	1	1	0	0
0	1	1	0	0	0	0	0	0	0	0
1	1	1	0	1	1	1	1	1	1	0
0	1	1	1	0	1	0	0	1	0	1
1	1	1	1	0	1	1	0	1	1	1
0	1	0	0	X	X	X	X	X	X	X
1	1	0	0	X	X	X	X	X	X	X
0	1	0	1	X	X	X	X	X	X	X
0	1	0	1	X	X	X	X	X	X	X

Table 4: State transition table - D flip-flops

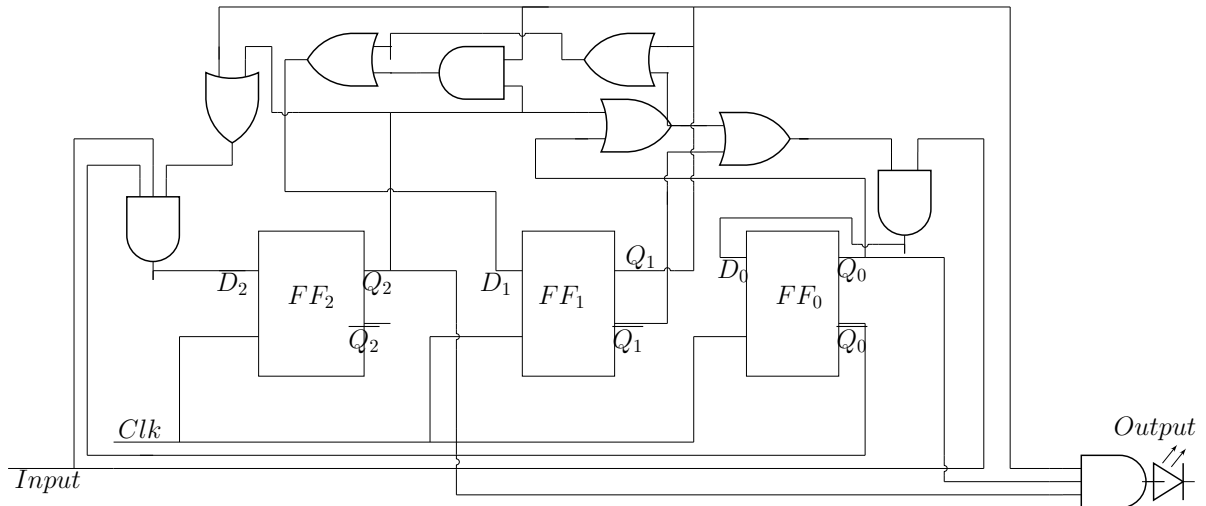


Figure 2: Circuit diagram

## 8 Observation

- The simulated diagram is attached herewith -

State	Logic
$D_2$	$D\overline{Q_0}(Q_1 + Q_2)$
$D_1$	$D(Q_0 + Q_1 + Q_2) + Q_1Q_0$
$D_0$	$D(Q_0 + Q_2 + \overline{Q_1})$
$O$	$Q_0Q_1Q_2$

Table 5: Logic - D flip-flops

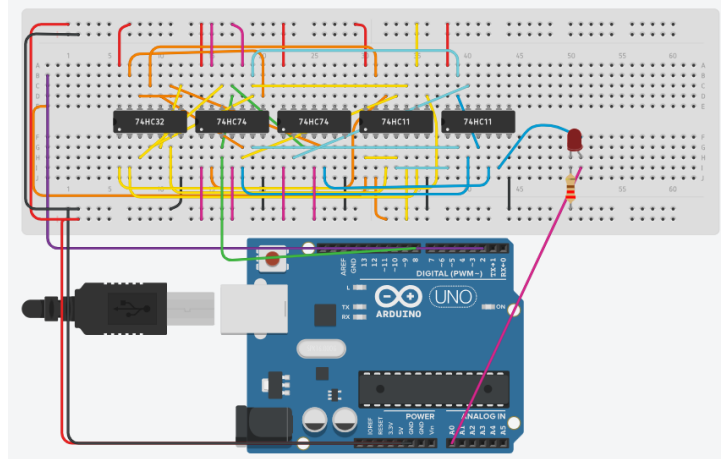


Figure 3: Simulated diagram

- It can be seen that the LED glows 4 times, in an interval of 3 seconds for the bit sequence **11011011011011** and 5 seconds for the first time to glow, in one cycle.
- This can be explained by the nature of the functioning of the Moore machine. When the circuit reaches  $S_5$ , the LED lights up, which can be seen from the circuit diagram.

## 9 Result

Hence, the sequence detector circuit has been constructed using logic gates and D-flip-flops, by a finite state machine ( FSM ) .